

國 立 宜 蘭 大 學

102 學年度研究所碩士班考試入學

電路學試題

(電機工程學系碩士班)

准考證號碼：

---

《作答注意事項》

1. 請先檢查准考證號碼、座位號碼及答案卷號碼是否相符。
2. 考試時間：100 分鐘。
3. 本試卷共有五題，共計 100 分。
4. 請將答案寫在答案卷上。
5. 考試中禁止使用大哥大或其他通信設備。
6. 考試後，請將試題卷及答案卷一併繳交。
7. 本試卷採雙面影印，請勿漏答。
8. 本考科可使用非程式型（不具備儲存程式功能）之電子計算機。

1. For the circuit in Fig. 1, find  $I$  and  $I_1$ . (20%)

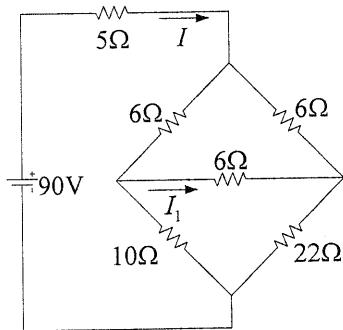


Fig. 1

2. For the circuit in Fig. 2,

(a) Find the Thevenin equivalent circuit with respect to the terminals  $A, B$ . (15%)

(b) Find the maximum average power delivered to  $R_L$ . (5%)

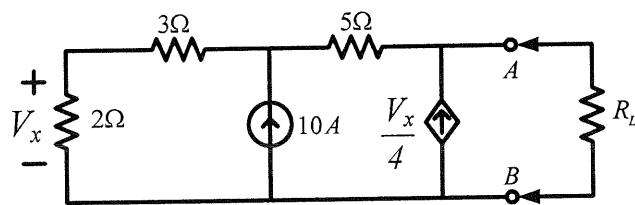


Fig. 2

3. Assume the OPA in the circuit of Fig. 3 is ideal in which  $R = 10 \text{ k}\Omega$  and  $C = 10 \mu\text{F}$ .

(a) Find the transfer function of  $\frac{V_o(s)}{V_i(s)}$ . Let  $V_o(s)$  and  $V_i(s)$  be Laplace transform of  $v_o(t)$  and  $v_i(t)$ . (10%)

(b) If the input voltage  $v_i(t) = 10 \sin(t) \text{ V}$ , find the steady-state response of  $v_o(t)$ . (10%)

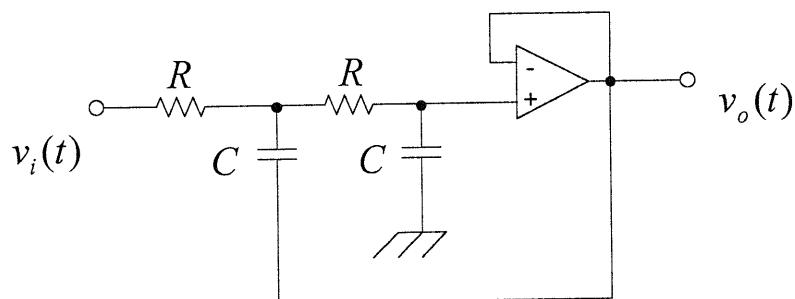


Fig. 3

背面尚有試題

4. The switch moves from  $a$  to  $b$  at  $t = 0$  second. Find the voltage  $v(t)$  for  $t \geq 0$ . (20%)  
(PS: Before  $t = 0$ , the circuit has reached steady state.)

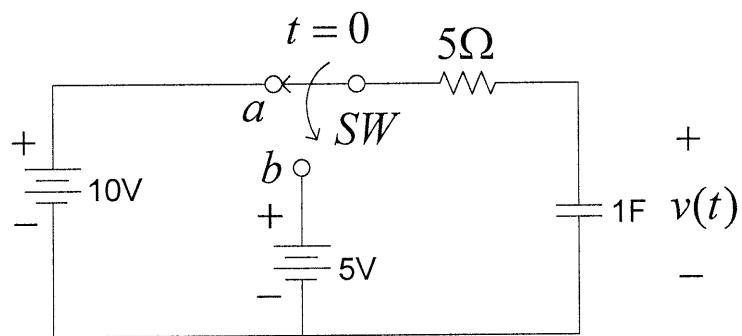


Fig. 4

5. For the circuit in Fig. 5, find the transfer function of  $\frac{V_2(s)}{V_1(s)}$ . Let  $V_1(s)$  and  $V_2(s)$  be Laplace transform of  $V_1$  and  $V_2$ . (20%)

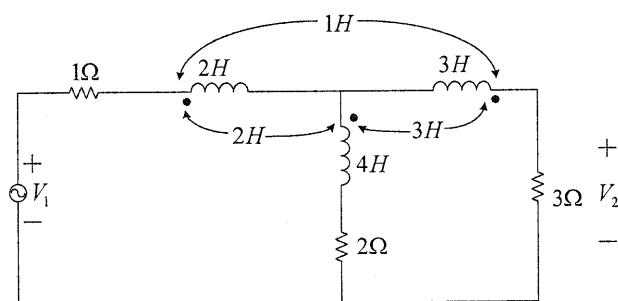


Fig. 5