

國立宜蘭大學  
九十八學年度轉學招生考試

(考生填寫)  
准考證號碼：


電 路 學 試 題

---


《作答注意事項》

1. 請先檢查准考證號碼、座位號碼及答案卷號碼是否相符。
2. 考試時間：80 分鐘。
3. 本試卷共有 5 題，一題 20 分，共計 100 分。
4. 請將答案寫在答案卷上。(限用藍或黑色鋼筆、原子筆作答)
5. 考試中禁止使用大哥大或其他通信設備。
6. 考試後，請將試題卷及答案卷一併繳交。
7. 本試卷採雙面影印，請勿漏答。

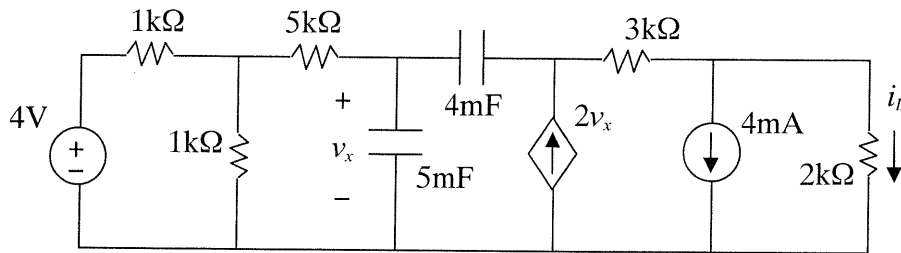
1. (20%) Under dc condition, determine the load current  $i_L$  and the energy stored in the 5mF capacitor.



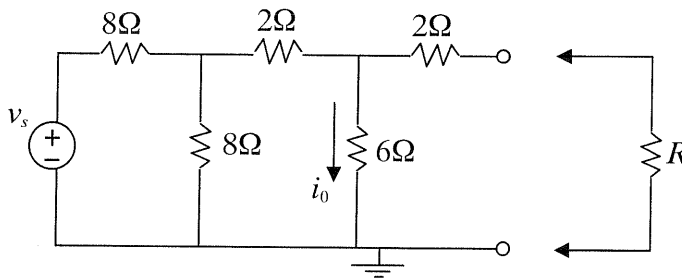
2. (20%) (a) When the load  $R$  is not connected, the current through 6Ω resistor is  $i_0=1A$ . Determine the source voltage  $v_s$ . (b) If the load  $R$  is connected, what is the maximum power can be transferred to  $R$ ?



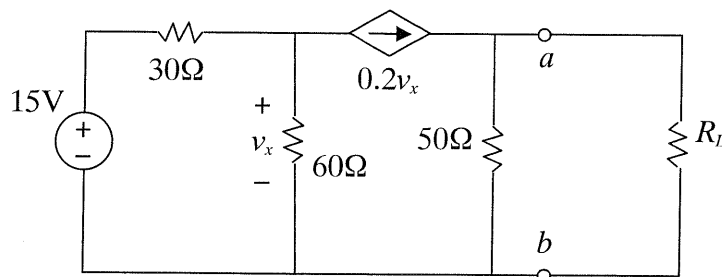3. (20%) Find the Norton equivalent circuits with respect to terminals  $a$  and  $b$ .



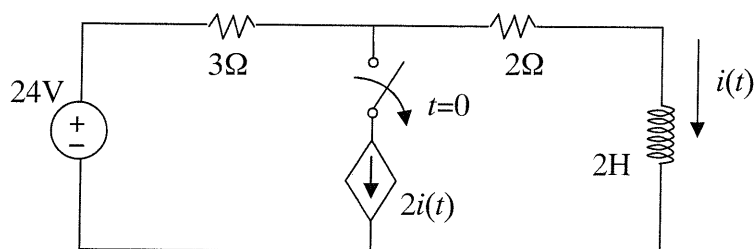4. (20%) Suppose that the switch has been closed for a long time and is opened at  $t=0$ . Determine the inductor current  $i(t)$  for  $t>0$ .



5. (20%) Consider the following third-order circuit with input voltage  $v(t)$ . Write the state equation  $\dot{\mathbf{x}}(t) = \mathbf{A}\mathbf{x}(t) + \mathbf{b}v(t)$ , where  $\mathbf{x}(t) = [x_1(t) \ x_2(t) \ x_3(t)]^T$  contains three state variables  $x_1(t)$ ,  $x_2(t)$  and  $x_3(t)$  shown in the circuit.

