

(1) Please explain the following keywords:

- (a) Forward active (for BJT operation) (5%)
- (b) Pinch-off (for FET) (5%)
- (c) LED (5%)
- (d) ECL (5%)
- (e) Early effect (for BJT) (5%)
- (f) EEPROM (5%)
- (g) Body effect (for MOS) (5%)
- (h) Slew rate (5%)

(2) Consider the circuit shown in Figure 1. Assume each diode cut-in voltage is $V_T = 0.6$ V. Find R_1, R_2, R_3 such that $I_{D1} = 0.2$ mA, $I_{D2} = 0.3$ mA, $I_{D3} = 0.5$ mA. (10%)

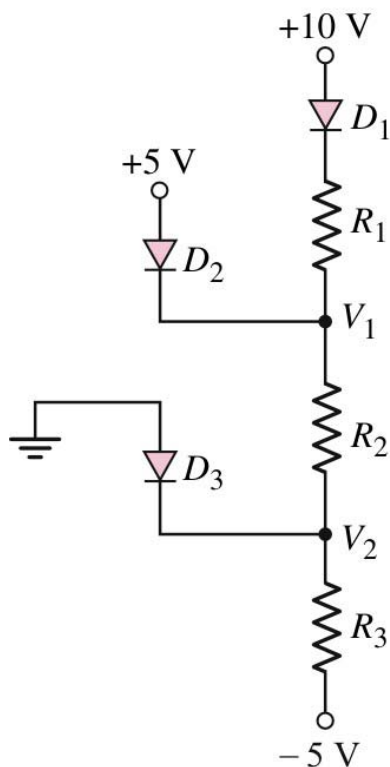


Figure 1

(3) Find the input resistance R_i for the circuits shown in Figure 2. The parameters of each transistor are $\beta = 100$ and $I_{CQ} = 0.26\text{mA}$. (10%) ($V_T = 26\text{mV}$)

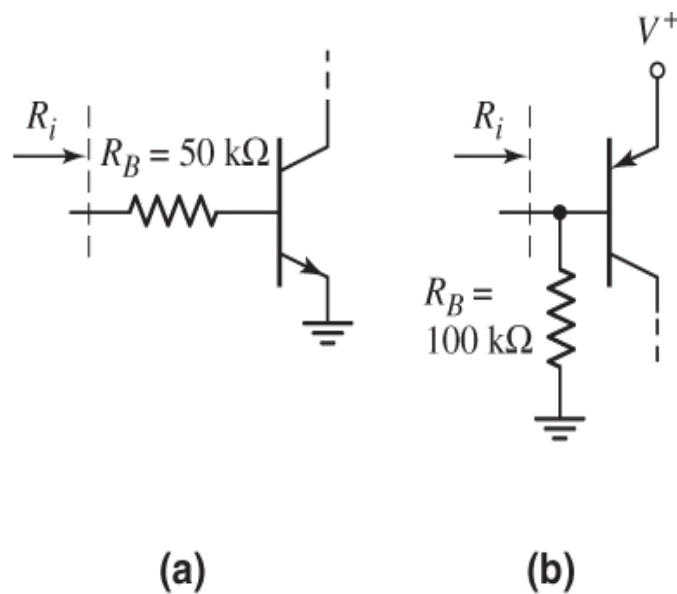


Figure 2

(4) What is the logic function implement by the circuit in Figure 3. (10%)

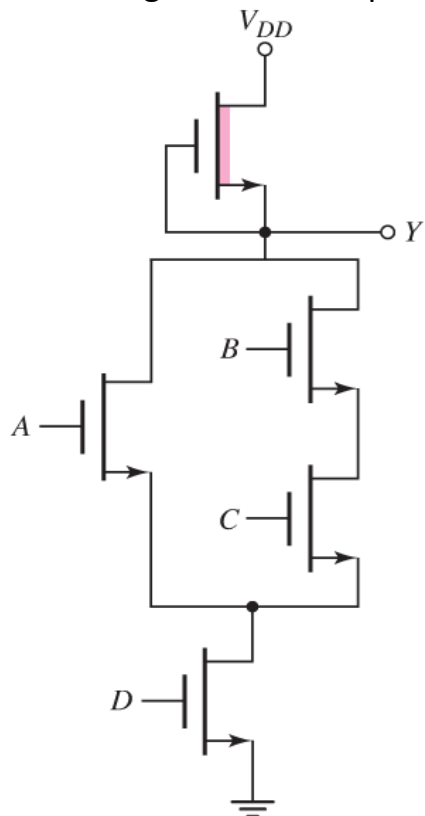


Figure 3

- (5) Find the unity-gain frequency f_T of an FET. The parameters of an n-channel MOSFET are $K_n = 3.14 \text{ mA/V}^2$, $V_{TN} = 0.4 \text{ V}$, $C_{gd} = 10 \text{ fF}$, and $C_{gs} = 30 \text{ fF}$. Assume the transistor is biased at $V_{GS} = 0.8 \text{ V}$. (where $K_n = \frac{W\mu_n C_{ox}}{2L}$) (10%)

- (6) Consider the circuit shown in Figure 4. Please show that the close-loop transresistance gain is given by (10%)

$$A_{zf} = \frac{v_o}{i_i} = \frac{+(A_Z + \frac{r_{\pi} R_C}{R_F})}{\left(1 + \frac{R_C}{R_F}\right)\left(1 + \frac{r_{\pi}}{R_F}\right) - \frac{1}{R_F}\left(A_Z + \frac{r_{\pi} R_C}{R_F}\right)}$$

where $A_Z = -g_m r_{\pi} R_C = -h_{FE} R_C$

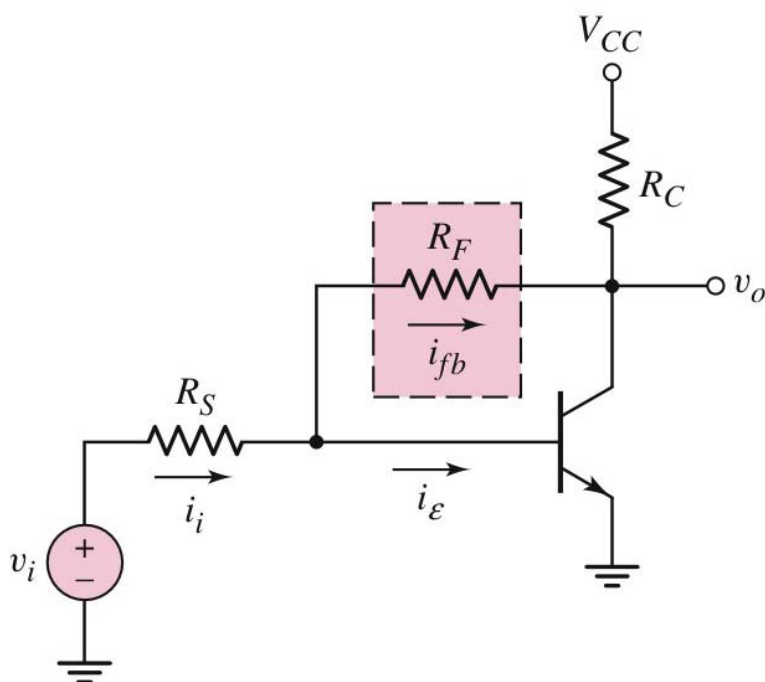


Figure 4

(7) For the amplifier in Figure 5, determine (a) the closed-loop voltage gain

$A_v = v_o/v_i$, (b) v_o for $v_i = 0.2\text{V}$. (10%)

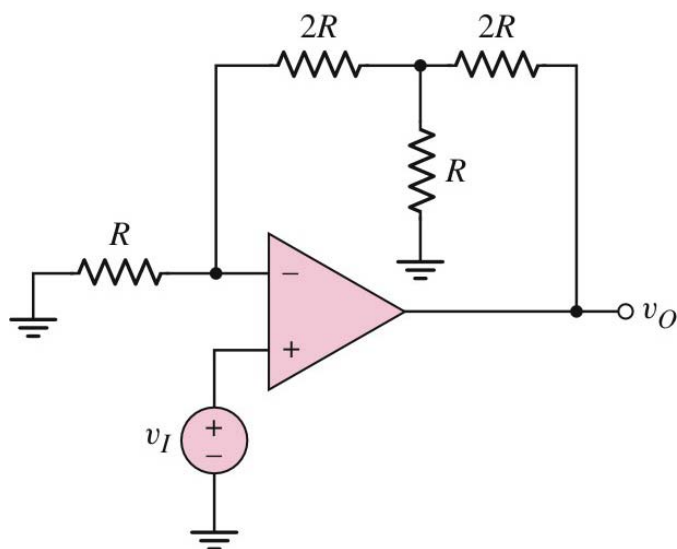


Figure 5