

1. For the circuit in Fig. 1, the NMOS transistor  $Q_1$  has  $V_t = 1V$ , and  $\mu_n C_{ox} = 20\mu A/V^2$ , and the PMOS transistor  $Q_2$  has  $V_t = -1V$ , and  $\mu_p C_{ox} = 10\mu A/V^2$ . Given  $(W/L)_1 = 2(W/L)_2$ . Find the value of  $V_m$ . (20%)

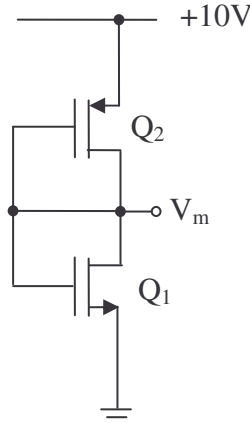


Fig. 1

2. Assume the op amp in Fig. 2 to be ideal. Find  $v_o$  in terms of the input voltages  $v_1$ ,  $v_2$  and  $v_3$ .  
Hint: use superposition. (10%)

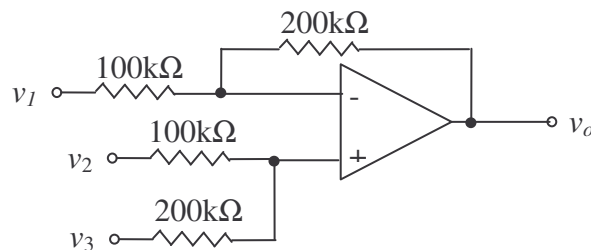


Fig. 2

3. For the circuit in Fig. 3, the *n*pn transistor  $Q_1$  has  $V_{BE} = 0.7V$  and the *p*np transistor  $Q_2$  has  $V_{EB} = 0.7V$ . Find the values of  $V_o$  for:  
(a)  $\beta = \infty$ . (10%)  
(b)  $\beta = 100$ . (10%)

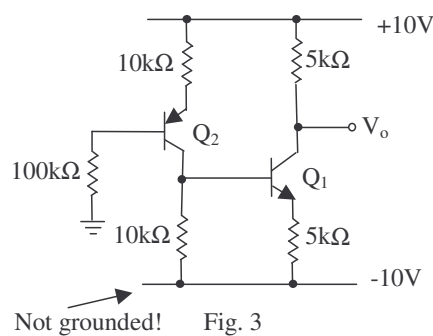


Fig. 3

4. Consider the cascode configuration of the differential amplifier shown in Fig. 4. Find the output resistance and the voltage gain of the circuit. (negligible body effect) (10%)

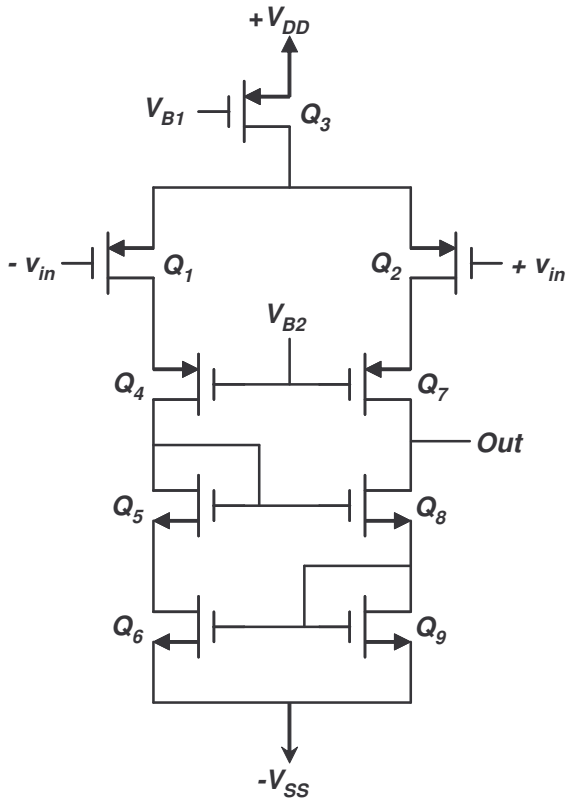


Fig. 4.

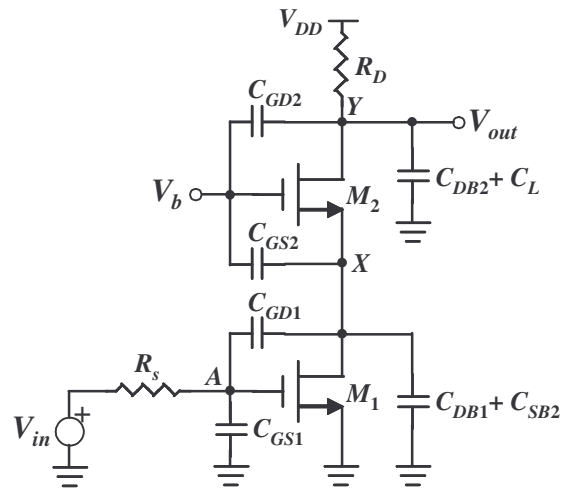


Fig. 5.

5. Consider the circuit shown in Fig. 5. Find the approximate poles of the three nodes A, X, and Y. (negligible channel-length modulation) (20%)
6. Find the closed-loop gain and the output impedance of the circuit shown in Fig. 6. (20%)

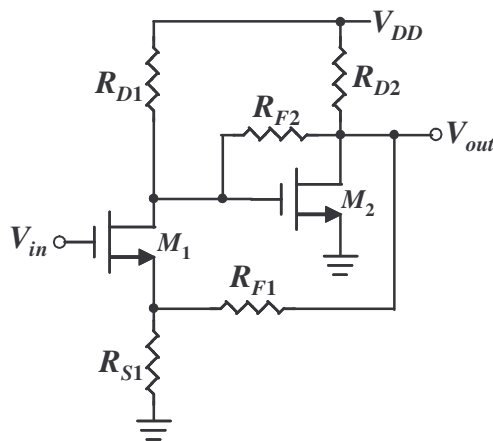


Fig. 6.