

- The circuit of Fig. 1 is a phase-shifting circuit. Assume that the OP Amp is ideal.
 - Derive the transfer function of this phase-shifting circuit. (10%)
 - Please Find R_i in Fig. 1 so that V_o will lag E_i by 90° . The frequency of E_i is 1 kHz. (5%)

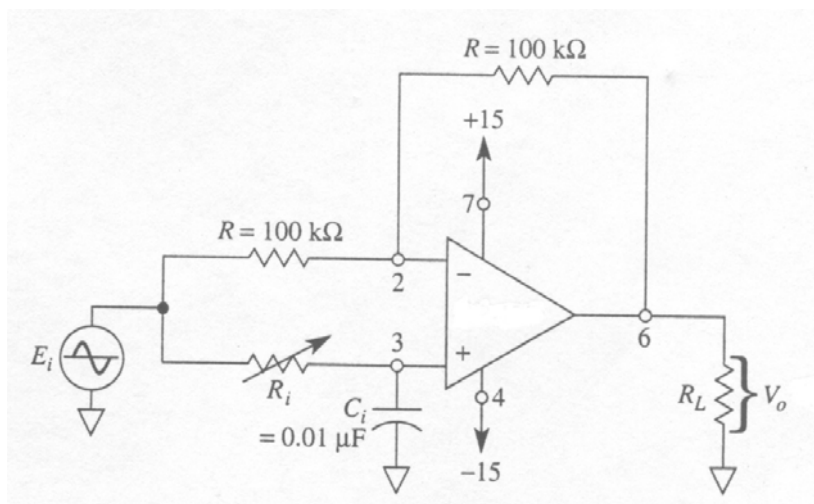


Fig. 1

- The circuit of Fig. 2 is an adder-subtractor. Assume that the OP Amp is ideal. Please find R_x in Fig. 2 so that its output is $V_{out} = -4V_1 - 2V_2 + 10V_3 + V_4$. (15%)

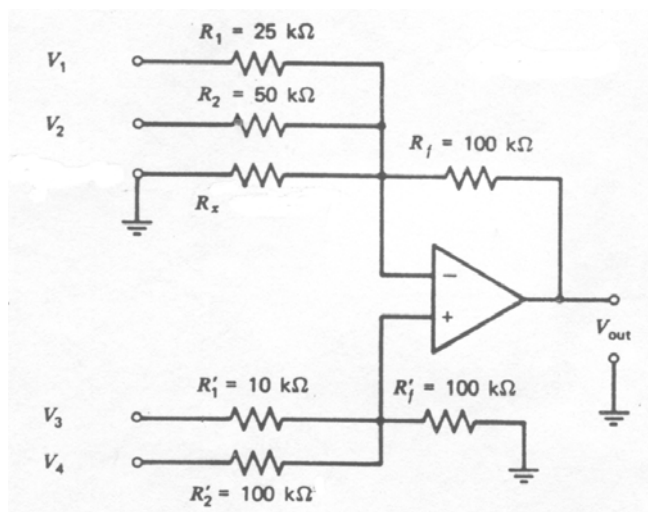


Fig. 2

3. A BJT with $\beta=100$ is used in Fig. 3 with the voltage $V_{BE} = 0.7V$.
- Determine the dc current I_{CQ} and the dc voltage V_E of the BJT. (5%)
 - Sketch the small signal equivalent circuit. (5%)
 - Find the voltage gain v_o/v_s and the input resistance R_{in} . (15%)

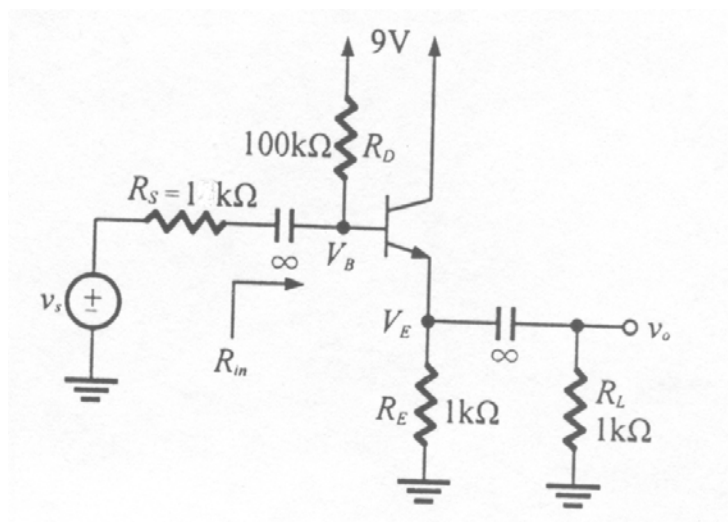


Fig. 3

4. For the circuit shown in Fig. 4, assume high β and BJTs having $V_{BE} = 0.7V$ at 1mA.
- Find the value of R that will result in $I_o = 10\mu A$. (10%)
 - For the design in (a) find the output resistance R_o , assuming $\beta=100$, $V_A = 100V$ and $V_T = 25\text{ mV}$. (10%)

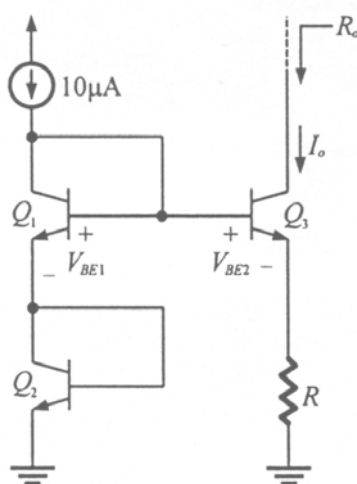


Fig. 4

5. For the circuit shown in Fig. 5, determine the small-signal voltage gain, $A_v = v_o / v_i$. Assume transistor parameters of $V_{TN} = 1\text{V}$, $K_n = 0.2 \text{ mA/V}^2$, and $\lambda = 0$ for M_1 and $\beta = 80$ and $V_A = \infty$ for Q_1 . (15%)

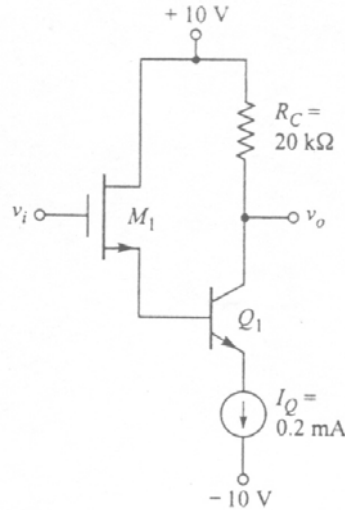


Fig. 5

6. For the circuit shown in Fig. 6, assume that the OP-AMPS are ideal. Determine the values of R_1 and R_2 so that the circuit will operate as a full-wave rectifier with a gain of 5. (10%)

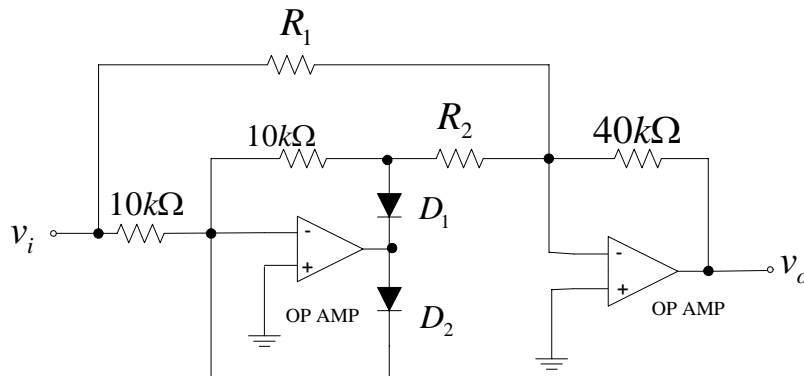


Fig. 6