

1. Find the Norton equivalent circuit of the circuit in Fig. 1 at terminals a-b. (15%)

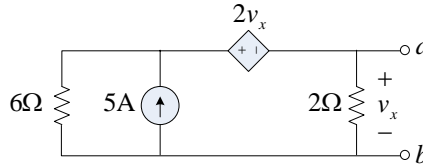


Fig. 1

2. The circuit in Fig. 2 is for a difference amplifier. Calculate  $v_1$ ,  $i_x$ , and  $v_o$ . (15%)

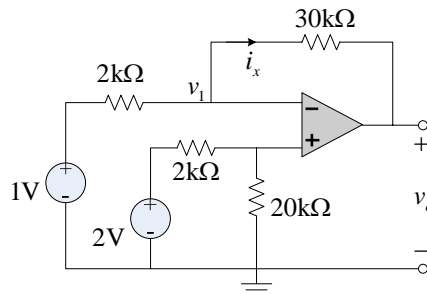


Fig. 2

3. The switch in Fig. 3 has been closed for a long time. It opens at  $t = 0$ . Find  $i(t)$  for  $t \geq 0$ . (20%)

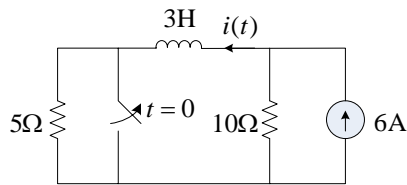


Fig. 3

4. For the circuit shown in Fig. 4. Find the steady state value of  $i(t)$ . (15%)

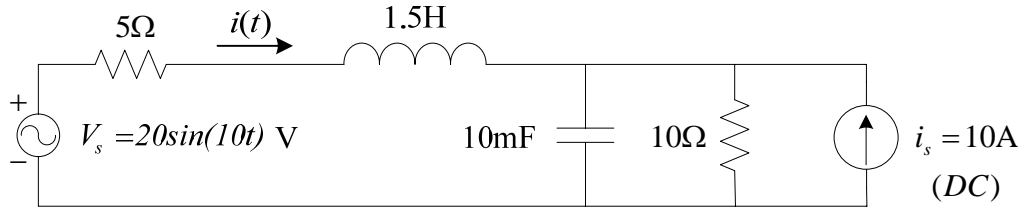


Fig.4

5. Assume the transformer in the circuit of Fig. 5 is ideal. Find the average power dissipated by the resistor  $R_2$ . (15%)

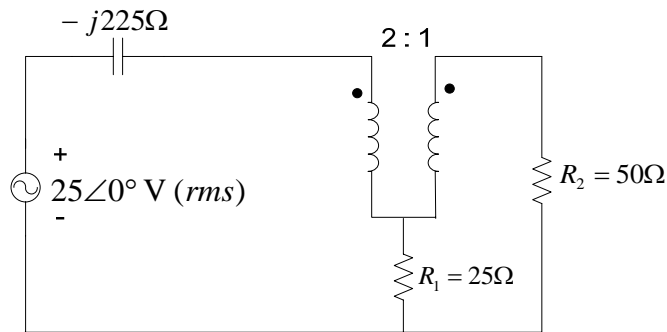


Fig. 5

6. Assume the OPA in the circuit of Fig. 6 is ideal in which  $R = 10\text{K}\Omega$  and  $C = 1\mu\text{F}$ .

(a) Find the transfer function of  $\frac{V_o(s)}{V_i(s)}$ . (10%)

(b) Find the steady-state response of  $v_o(t)$  if the input voltage  $v_i(t) = 5\sin(t)$  V. (10%)

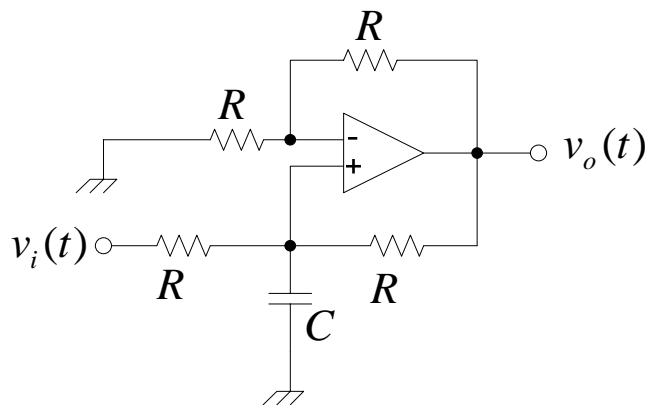


Fig.6